

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0000

Roll No.

--	--	--	--	--	--	--	--

B. Tech –

MODEL PAPER-2

FUNDAMENTALS OF Electronics Engineering

Time: 03:00 hrs

Total Marks: 70

- Note: (1) Attempt questions as per instructions given against them.
 (2) Be precise in your answer.

SECTION - A

Ques-1 Attempt all parts of this section :

(2X 7 =14)


- a. If α of transistor changes from 0.981 to 0.987, find the % change in β .
- b. What do you mean by Offset in OP_AMP. List the ideal characteristics.
- c. What do you mean by slew rate?
- d. A Ge Diode carries a current of 1mA at room temp. when forward bias of 0.15v is applied. Find the reverse saturation current.
- e. Convert the following:
 - i. $(3509)_{10} = (?)_{16}$
 - ii. $(54)_{10} = (?)_4$
- f. Convert the following in SOP or POS: $Y = AB + AC + BC$
- g. Draw the basic block dig of communication system.

SECTION- B

Quest- 2 Attempt any 3 parts of this section :


(7 X 3 =21)

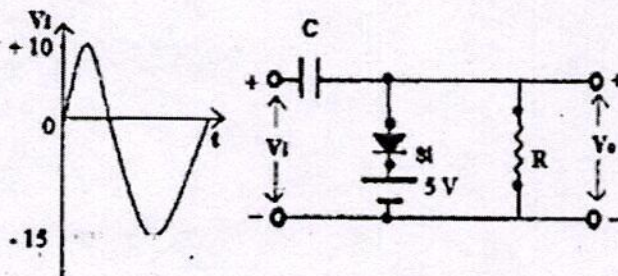- a. i. For the given clamper circuit determine the output voltage and draw the output waveform.



- ii. For a Half Wave Rectifier derive the expression of Ripple factor and TUF.
- i. Explain the working of JFET and explain its input output characteristics.
 - ii. Explain EMOSFET with input output characteristics.

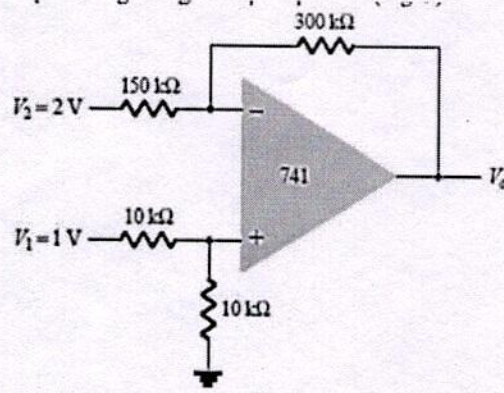- c. i. Explain the working of OP-amp as Integrator and differentiator.
 ii. Find the output of the given circuit :



- d. i. What do you mean by Universal Gates? Design the XOR and XNOR gate with the help of any 1 Universal gate.

ii.

a> Determine the value of x if $(193)_x = (623)_8$

b> Perform the following operation : $(756)_8 - (637)_8 + (725)_{16}$

- e. i. What do you mean by Modulation? Explain the need of modulation.

ii. The output voltage of transmitter is given by $300(1+0.5\sin 50t) \sin 2.14 \times 10^7 t$. This voltage is fed to a load of 600 ohm resistance. Determine:

i. Carrier Power ii> Modulating Frequency

iii. Total Power Delivered.

ii. What do you mean by Radar ? Explain the elements of Radar Communication. What are the applications of RADAR ?

- f. i. Explain the working of IoT. Advantages and disadvantages of IoT along with its applications.


ii

SECTION- C


Ques 3. Attempt all parts and 1 of each of section.

(7x 5 = 35)

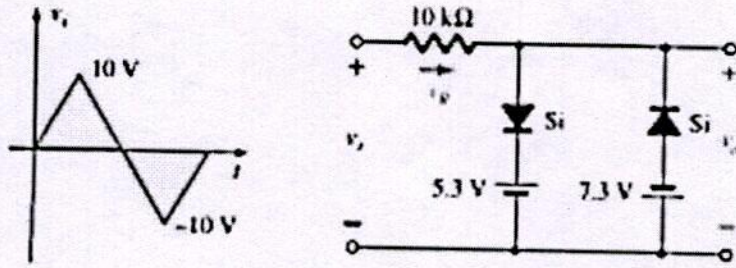- a. i. For the given network find the output voltage:



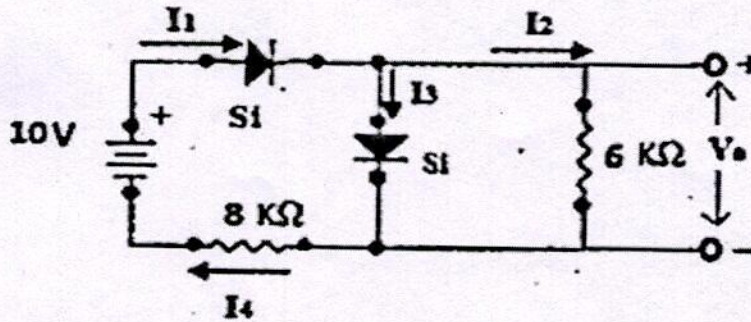- ii. Determine the currents I_1, I_2, I_3, I_4 and V_o for the network shown:



- a. i. Explain the working of Full wave Doubler, Tunnel Diode and LED.
- ii. Draw and explain the working of Zener Diode as a Shunt regulator. For the Regulator circuit if $R_s = 240 \text{ ohm}$, $V_z = 12 \text{ Volt}$, $R_L = 500 \text{ ohm}$, $V_{in} = 30 \text{ Volt}$, Calculate the value of Zener current, Load current and source current.
- b. i. Explain the working of Depletion MOSFET along with its VI characteristics.
- ii. Explain the working of Common emitter configuration along with its input output characteristics.
- c. i. Explain the working OP-Amp as an Inverting adder for 3 inputs.
- ii. Draw and explain the working of OPAMP as an integrator. Draw its input output characteristics.
- d. i. Define Amplitude modulation and derive the equation of AM wave.
- iii. Minimize the SOP expression given below using K-map.
- $$y = \sum m(1,3,7,11,12,15) + \sum d(0,2,5,8,14)$$